



Class: XI	Department: Computer Science	Date of submission:
Worksheet -2	Topic: Boolean Algebra	Note: for practice

1. Prove the Boolean Laws shown below using Truth Table.

a) $X + X'Y = X + Y$

b) $X + XY = X$


c) $X + YZ = (X + Y)(X + Z)$

2. Write a short note on Boolean Algebra explaining all the gates.


3. State and prove De Morgan's Theorems using truth table

4. Convert the following logic gate circuit into a Boolean expression. (Write the Boolean expression for the given circuits)


a)

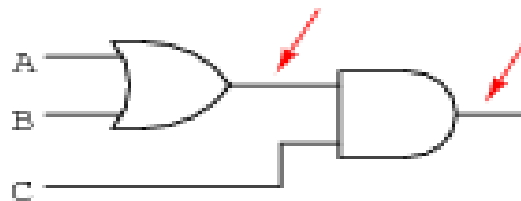

b)

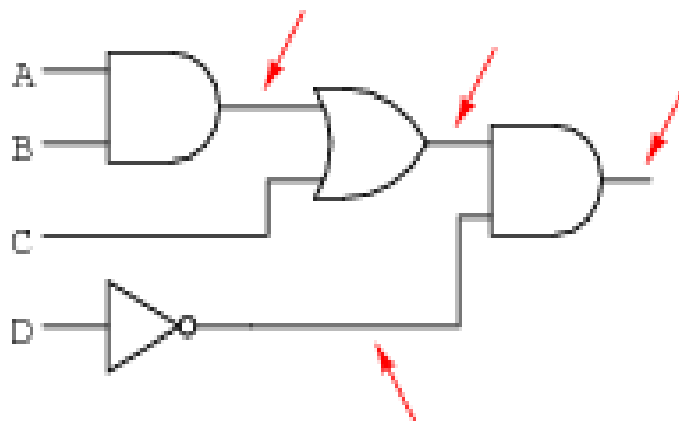

c)

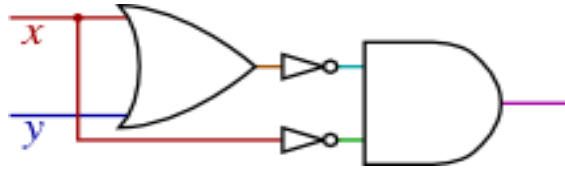

5. Draw a circuit diagram and truth table for the given Boolean Expressions:

a) $y = A + C \cdot B + C' \cdot A' + B + C$

b) $F = A' \cdot B \cdot C \cdot (A + D)'$


c) $F = A \cdot B' + C' \cdot D$

d) $F = (U \cdot V') + (U' \cdot W')$

e) $F = A \cdot B + A \cdot C' + B' \cdot A' \cdot C$

f) $F = (X + Y) \cdot (X' + Z') \cdot (Y + Z)$

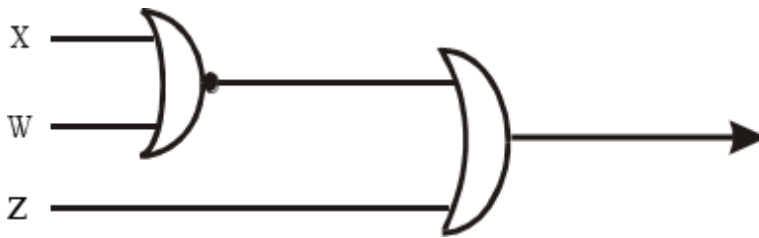6. Obtain logic expression for the following logic circuit:



7. Write the Boolean expression for the given below logic circuit.

